
Name:	Country Code:

Task(example)

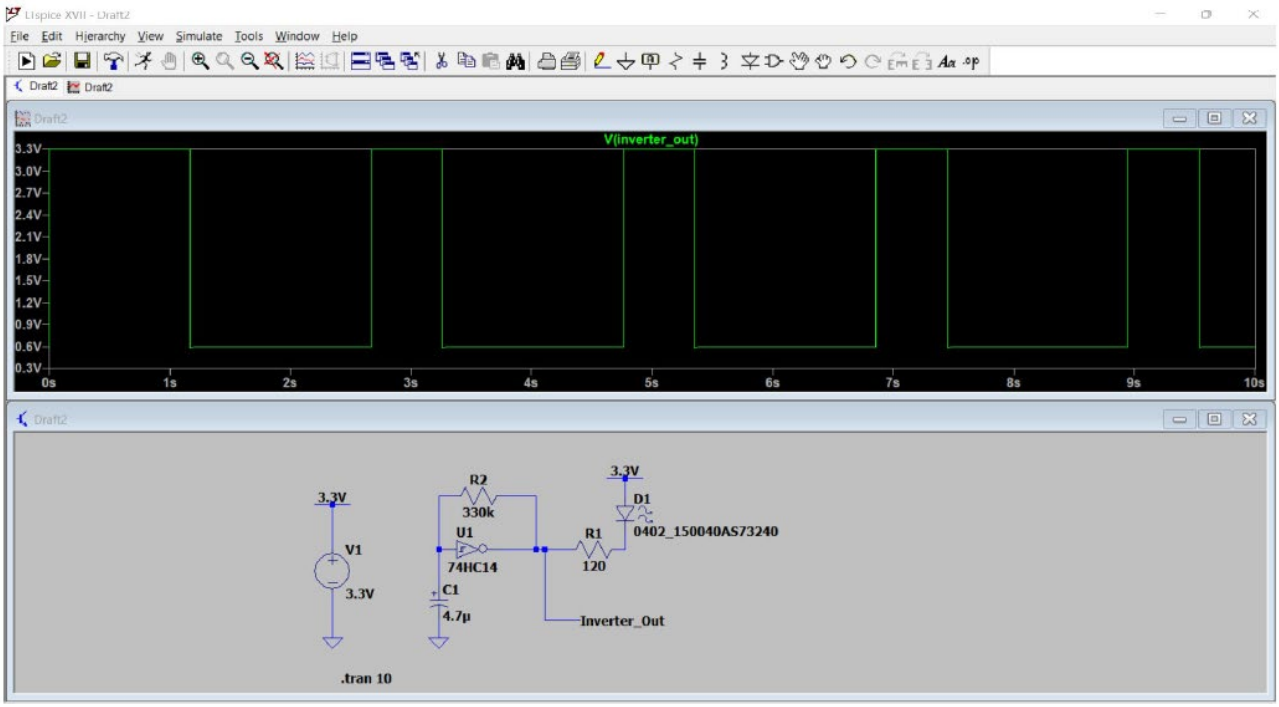

© WorldSkills International

Name：	Country Code：

Task1 Constant current charging circuit （LTspice)

Calculations:

Screen Capture 1 goes here.

© WorldSkills International

Name：	Country Code：

Task2 Voltage regulator （LTspice)

Calculations:

Screen Capture 1 goes here.

Screen Capture 2 goes here.

© WorldSkills International

Name:	Country Code:

Task3A Pre-amplifier circuit (LTspice)

Calculations:

Screen Capture 1 goes here.

Screen Capture 2 goes here.

© WorldSkills International

Name：	Country Code：

Task3B Current amplification circuit （LTspice)

Calculations:

Screen Capture 1 goes here.

© WorldSkills International

Name：	Country Code：

Task4 Current sampling circuit （LTspice)

Calculations:

Screen Capture 1 goes here.

© WorldSkills International

Name:	Country Code:

Task5 Drive circuit (LTspice)

Calculations:

Screen Capture 1 goes here.

© WorldSkills International